
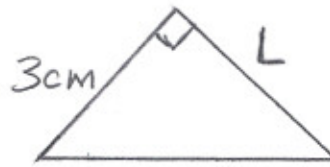


2.)

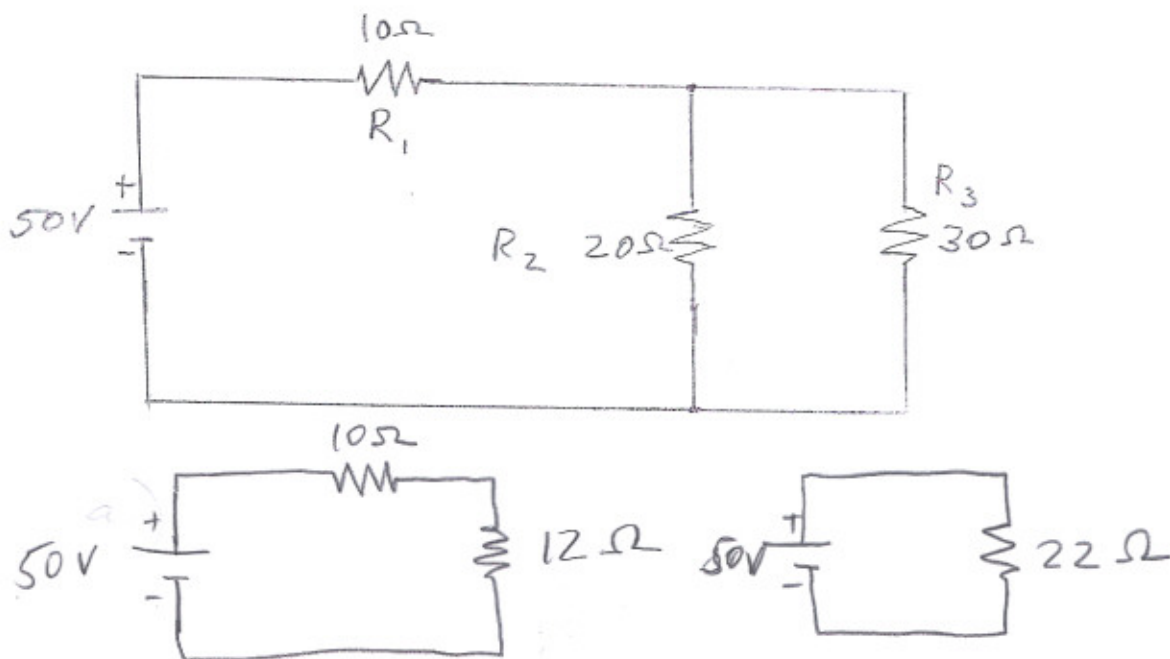

A solid copper bar 2.5 m in length has a cross-section as shown above. The bar is used as a grounding conductor designed to carry 100 A of current with a power consumption of 0.5 W. What is the length of side L of its cross-section in centimeters?

5. For the circuit shown below,
- how much current flows through each resistor?
 - how much voltage is across each resistor?
 - what is the equivalent resistance?
 - how much power does the battery supply to the circuit?



- $R_1 \rightarrow 2.27 \text{ A}$ $R_2 \rightarrow 1.36 \text{ A}$ $R_3 \rightarrow 0.91 \text{ A}$
- $R_1 \rightarrow 22.7 \text{ V}$ $R_2 \rightarrow 27.3 \text{ V}$ $R_3 \rightarrow 27.3 \text{ V}$
- $R_{eq} = 22 \Omega$
- $\frac{(50\text{V})^2}{22\Omega} = 114 \text{ W}$

2. The power to your home is suddenly disconnected. You talk a neighbor into allowing you to plug an extension cord into their house. You power a 100 W at 120 V lightbulb so that you can see to complete your physics homework. The extension cord is 25 m long and has a pair of 16 ga (0.00129032 m diameter) copper wires.

- What is the resistance of the bulb at 120 V?
- How much energy does the bulb use in 1 hour of time?
- How much power is dissipated through the extension cord? (Assume that the potential difference across the bulb is 120 V.)

$$a.) \quad P = \frac{V^2}{R} \quad R = \frac{V^2}{P}$$

$$R = \frac{(120V)^2}{(100W)} = \boxed{144 \Omega}$$

$$b.) \quad 100W = 100 \frac{J}{s}$$

$$\frac{100J}{s} \times 3600s = \boxed{3.6 \times 10^5 J}$$

$$c.) \quad R = \frac{\rho l}{A} \quad \left(\frac{(1.7 \times 10^{-8} \Omega \cdot m)(25m)}{\frac{\pi (0.00129032m)^2}{4}} \right) =$$

$$R = 3.25 \times 10^{-1} \Omega$$

$$I = 8.33 \times 10^{-1} A$$

$$P_{\text{cord}} = 2(I^2 R)$$

$$= \boxed{0.45 W}$$